

Harry Langford hjel2

Paper 2

Question 1.

a) we could either use:

$$M = 0, N = 0$$

or

$$M = 1, N = 1$$

Q	Inputs MN	Current State		Next	
		Q		Q'	
0	00	0		0	
0	01	0		1	
0	10	0		0	
0	11	0		1	
1	00	1		0	
1	01	1		1	
1	10	1		1	
1	11	1		0	

c) A Moore machine is appropriate since the output is only dependant on state

d) Let there be 3 flipflops F_2, F_1, F_0 where F_2 is the MSB

Current State		Next State	
F_2, F_1, F_0		F_2, F_1, F_0	
000		001	
001		010	
010		011	
011		100	
100		101	
101		110	
110		000	

Harry Langford hjel 2

e) Current Let M_i, N_i be the inputs for F_i

Current State	Next State	Controls
$F_2 F_1 F_0$	$F_2 F_1 F_0$	$M_2 N_2$ & $M_1 N_1$ & $M_0 N_0$
000	001	00 1 0 1 1
001	010	00 1 1 1 1
010	011	00 1 0 1 1
011	100	01 1 1 1 1
100	101	01 1 0 1 1
101	110	01 1 1 1 1
110	000	00 1 0 1 0

f) For the inputs M_i : all M_i are either 0 or 1. So no logic is needed to compute them. So I will not draw K-maps for them.

N_2	$F_2 F_1$	
	00 01 11 10	$N_2 = F_2 \bar{F}_1 + F_1 F_0$
0	0 0 0 1	$M_2 = 0$
1	0 1 0 1	

~~$N_2 = F_2 \bar{F}_1 + \bar{F}_2 F_1 F_0$ $M_2 = 0$~~

N_1	$F_2 F_1$	
	00 01 11 10	
0	0 0 1 0	
1	1 1 0 1	

~~$N_1 = \bar{F}_2 \bar{F}_0 + \bar{F}_1 F_0 + F_2 F_1 \bar{F}_0$~~

$$N_1 = F_0 + F_2 F_1$$

$$M_1 = 1$$




Harry Langford hjel2

N_0	$F_2 F_1$			
	00	01	11	10
0	1	1	0	1
F_0	1	1	x	1

$$N_0 = \overline{F_2} + \overline{F_1}$$

$$M_0 = 1$$

v)

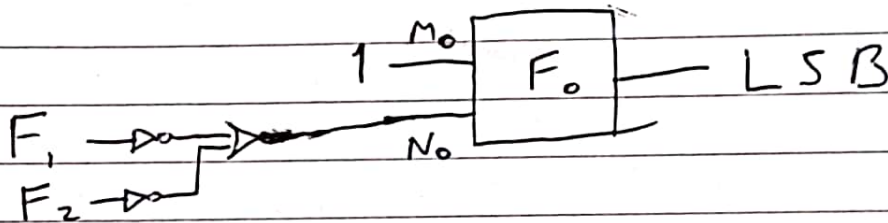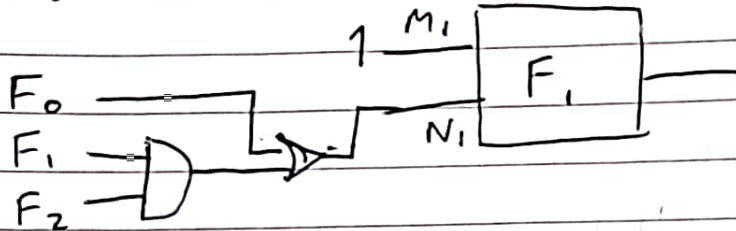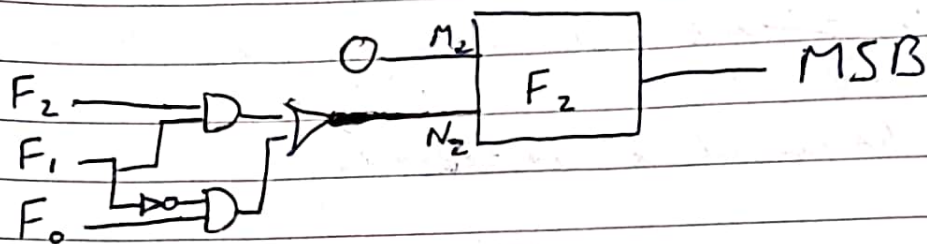

Some of these circuits could be simplified with NAND and NOR. This would speed them up.

But for clarity I've not included this:

i.e

$$N_0 = F_1 \text{ NAND } F_2$$

$$N_2 = (F_2 \text{ NAND } F_1) \text{ NAND } (\overline{F_1} \text{ NAND } F_0)$$

Harry Langford hje12

iv) The only invalid state is 111.

$$\text{If } F_2 F_1 F_0 = 111,$$

~~the next state is 1~~

$$M_2 = 0, N_2 = 1 \Rightarrow F_2' = 1$$

$$M_1 = 1, N_1 = 1 \Rightarrow F_1' = 0$$

$$M_0 = 1, N_0 = 0 \Rightarrow F_0' = 1$$

So the circuit will enter go to 101 --
a valid state.

So the circuit is self starting.